

# SC1005 Digital Logic

## Tutorial 9

Q1. (a) Explain what is wrong with the following code for a counter, and correct it:

```
module countwrong (input clk, rst, output reg [5:0] cnt_out);
```

```
    always@(posedge clk)
    begin
        cnt_out <= cnt_out + 1'b1;
    end
endmodule
```

the block's behaviour happens all the time when it should only happen at the clock rising edge

(b) The following combinational module is to be converted into a synchronous module. Add a register after each combinational stage in the original description, by rewriting the module using only a single synchronous always block:

```
module arch1 (input [6:0] a, b, output [13:0] total);
```

```
    wire [6:0] int1;
```

```
    assign int1 = a + b;
    assign total = int1 * int1;
```

```
endmodule
```

```
module arch1(input [6:0] a,b, rst, clk,
              output reg[13:0] total);
```

```
    wire [6:0] int1;
```

```
    always@(posedge clk)
```

```
    begin
```

```
        if (rst)
            total <= 14'd0;
```

```
        else
```

```
            int1 <= a + b;
```

```
            total <= int1*int1;
```

```
        end
```

```
    endmodule
```

Q2

A monitoring circuit has an input, *evnt*, that is high whenever a certain condition is met. It has an internal counter that counts the number of cycles in which *evnt* is high. When this count exceeds a threshold, determined by the 6-bit *thresh* input, it sounds an alarm by asserting the alarm output and stops the counter. The human operator can then check for problems and reset the system by asserting *rst*. Design a Verilog module that implements this circuit. (Hint: alarm should be a combinational circuit determined from the count value and threshold. It can be used to determine whether or not the counter counts in any given cycle).

Q3. (a) Write a Verilog description of a 5-bit binary counter that counts up to 20 and then wraps round to zero.

(b) Modify the counter in (a), adding a new 5-bit input, *countmax*. The counter should now wrap around at the *countmax* value.

(c) Write a Verilog module that implements a 6-bit counter that counts down from an initial value. The initial value should be loaded on reset from a 6-bit input, *start\_val*.