Answers

1. (a) T: True/asserted F: False/negated

| driver_present | buckled_up | ignition_on | warning_light |
|----------------|------------|-------------|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 (T) | 0 (F) | 1 (T) | 1 (T) |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

- (b) warning_light = (driver_present) (buckled_up)' (ignition_on)
- 2. (a) T: True/asserted F: False/negated

| driver_present* | buckled_up* | ignition_on* | warning_light* |
|-----------------|-------------|--------------|----------------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 (T) | 1 (F) | 0 (T) | 0 (T) |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

- (b) warning_light* = driver_present* + (buckled_up*)' + ignition_on*
- 3. (a) T: True/asserted F: False/negated

| driver_present* | _present* buckled_up* ignition_on | | warning_light | |
|-----------------|-----------------------------------|-------|---------------|--|
| 0 | 0 | 0 | 0 | |
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 0 | |
| 0 (T) | 1 (F) | 1 (T) | 1 (T) | |
| 1 | 0 | 0 | 0 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 0 | |

(b) warning_light = (driver_present*)' (buckled_up*) (ignition_on)
or warning_light = [driver_present* + (buckled_up*)' + ignition_on']'

Page 1 ©2021 NTU

4. F=1 when A=1 or C*=0 but not both; and B=0 or D*=1 but not both.

| Α | В | C* | D* | F |
|---|---|----|----|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$F(A,B,C^*,D^*) = \sum_{i=1}^{n} m(0, 5, 10, 15)$$

Active-high signals: True (asserted) when the signal is high

Active-low signals: True (asserted) when the signal is low

Page 2 ©2021 NTU