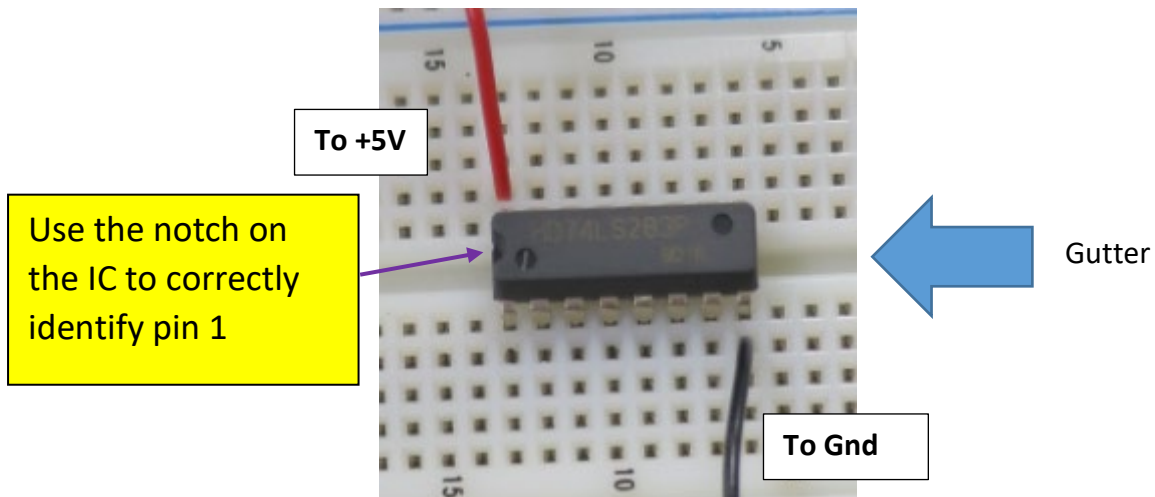



SC1005 Lab experiment 2 circuit connection guide

Different colour wires (they are the same functionally) are usually **used to make circuit connections** easier to trace. Students are encouraged to **follow the wire colours** suggested in this guide so that it is easier to trace the logic signals as well as to troubleshoot in the event the connected circuit does not function as expected.



1. Mount the **IC 74LS283** (4-bit adder) firmly on the breadboard across the gutter and connect its **Vcc** (pin 16, **red wire**) and **Gnd** (pin 8, **black wire**) to **5V** and **0V** respectively.




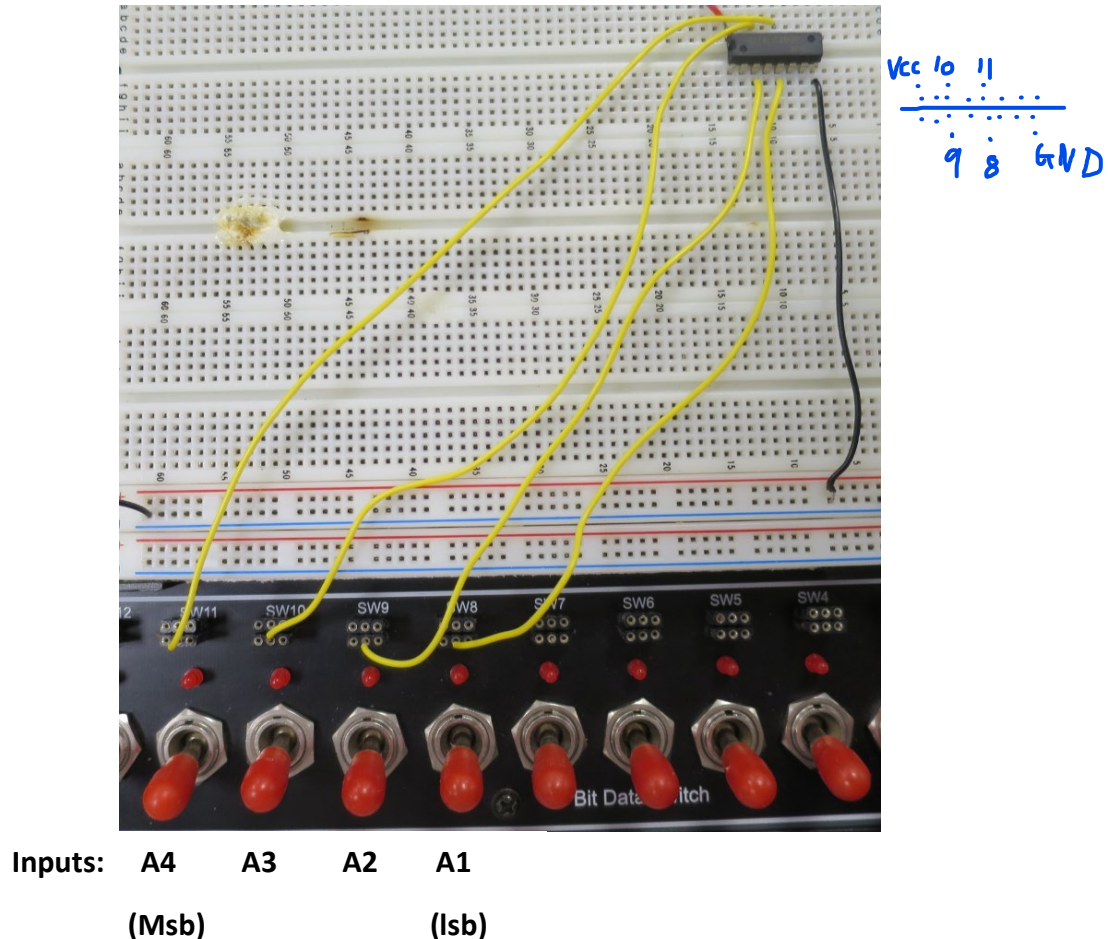
2. Connect the **input** pins A4 (msb), A3, A2, A1(lsb) to a **toggle switch** each (**yellow wires**).



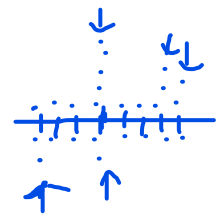
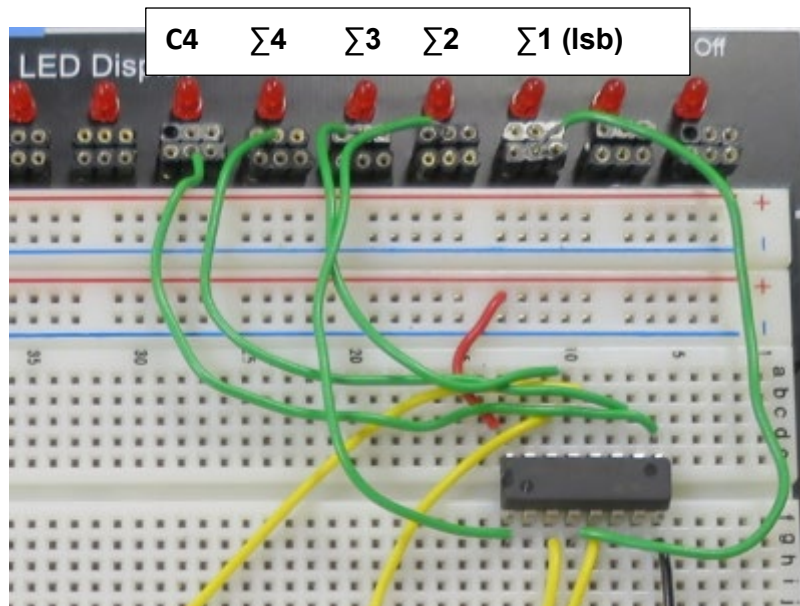
3. Connect the **output** pins C4, $\Sigma 4$ (msb), $\Sigma 3$, $\Sigma 2$, $\Sigma 1$ (lsb) to an LED each (**green wires**).



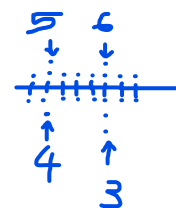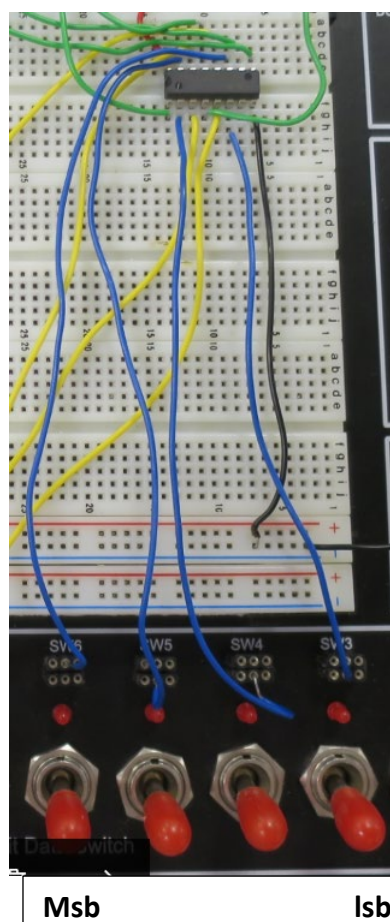4. Connect the **input** pins B4 (msb), B3, B2, B1 (lsb) to a toggle switch each (**blue wires**).




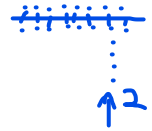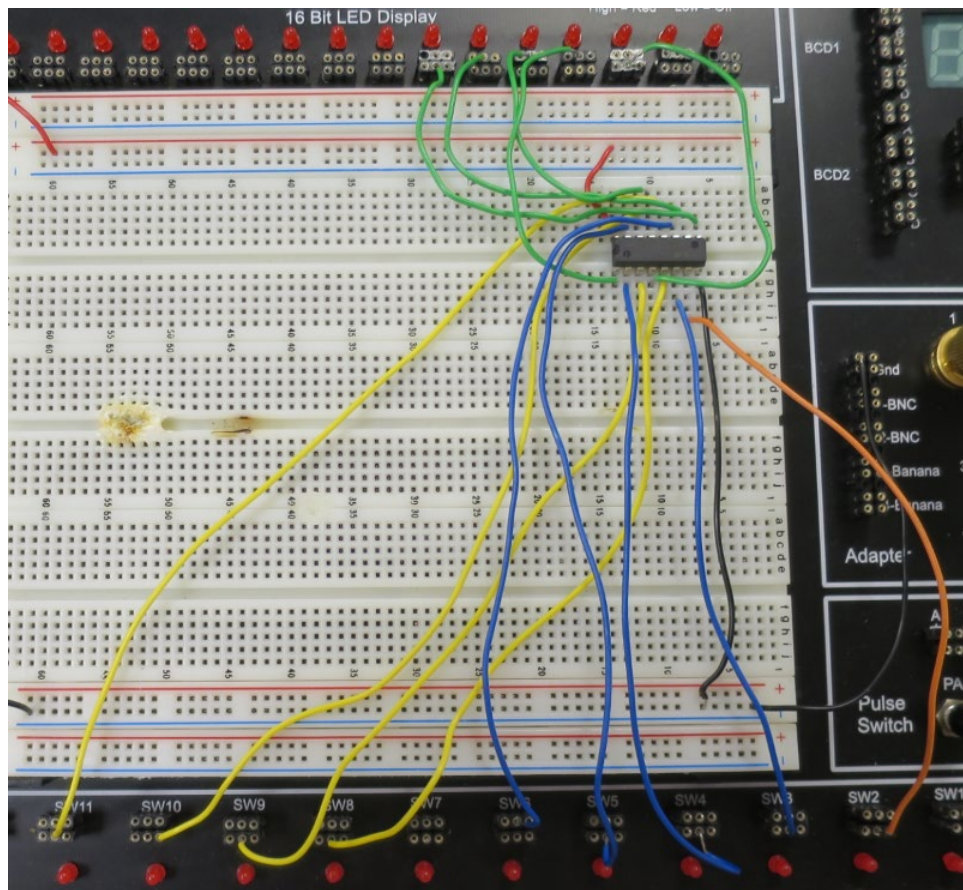5. Connect C0 (Carry input) to a toggle switch (orange wire).



6. Power up the circuit and test it out for arithmetic addition. This figure shows the largest addition result that can be produced by the 4-bit adder.


Outputs: C4 Σ 4 Σ 3 Σ 2 Σ 1

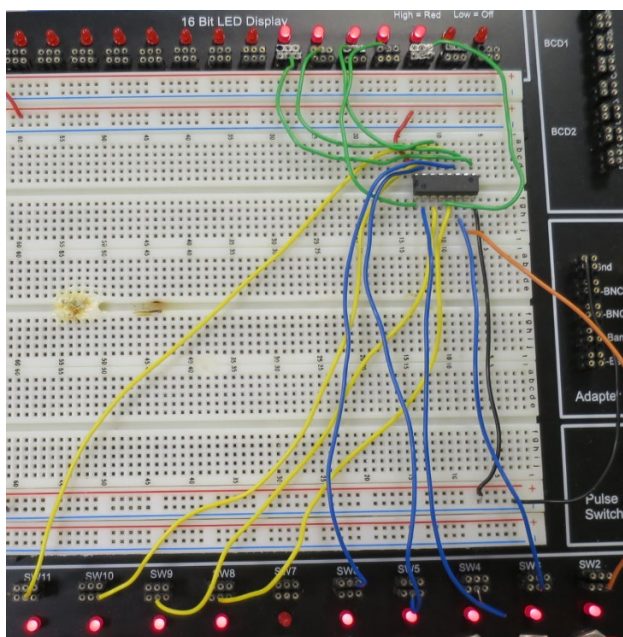

$$\begin{array}{r}
 1 \\
 1\ 1\ 1\ 1 \\
 +\ 1\ 1\ 1\ 1 \\
 \hline
 =\ 1\ 1\ 1\ 1\ 1
 \end{array}$$


Inputs: A4 A3 A2 A1 B4 B3 B2 B1 C0

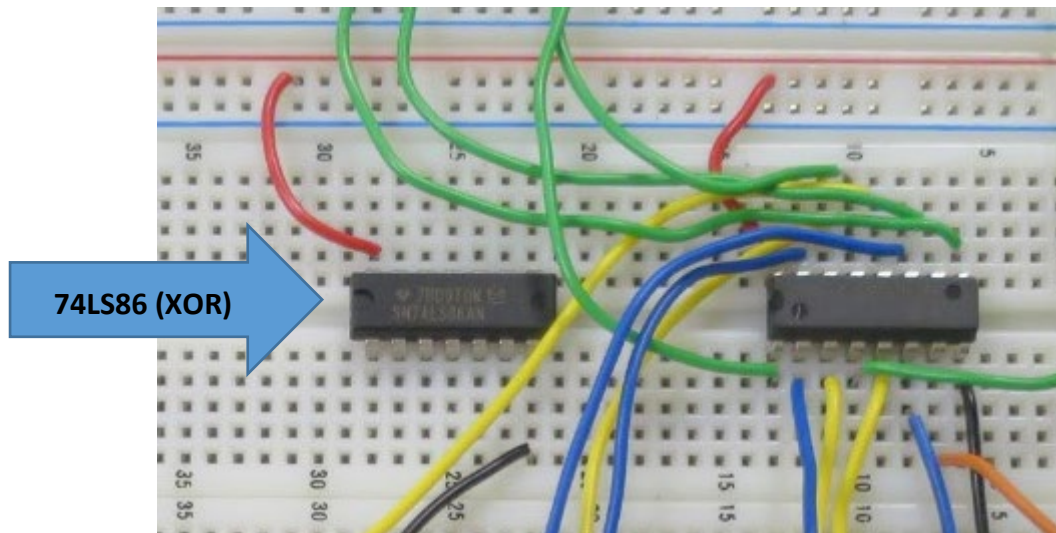7. **Power off the circuit board.** Mount the **74LS86 (quad-XOR)** IC and connect its **Vcc** and **Gnd** pins to **5V (red wire)** and **0V (black wire)** respectively.



8. **Disconnect the toggle switches from B4, B3, B2, B1 of the 74LS283 (4-bit adder) and connect them to the 74LS86 (quad-XOR) instead** (i.e. the lower end of each **blue** wire remains connected to the toggle switch, but the upper end is connected to the 74LS86 instead of the 74LS283).

Change this
end of each
blue wire

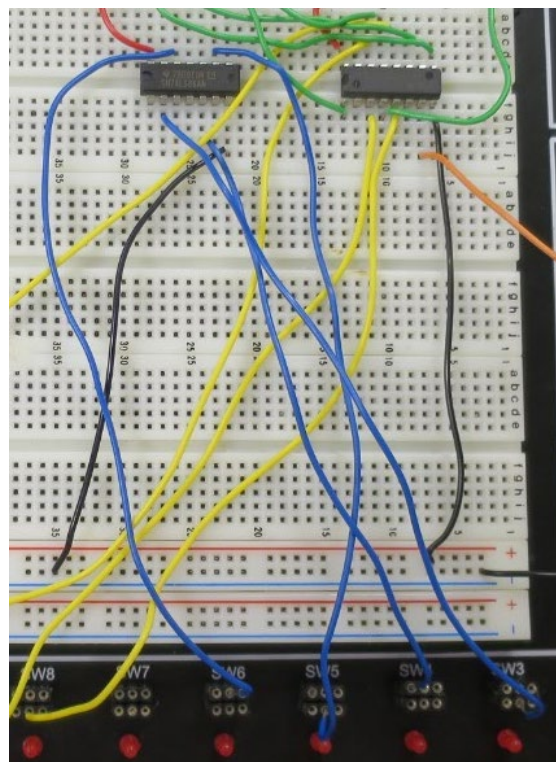



See blue

No change to
this end of each
blue wire



Msb

Isb

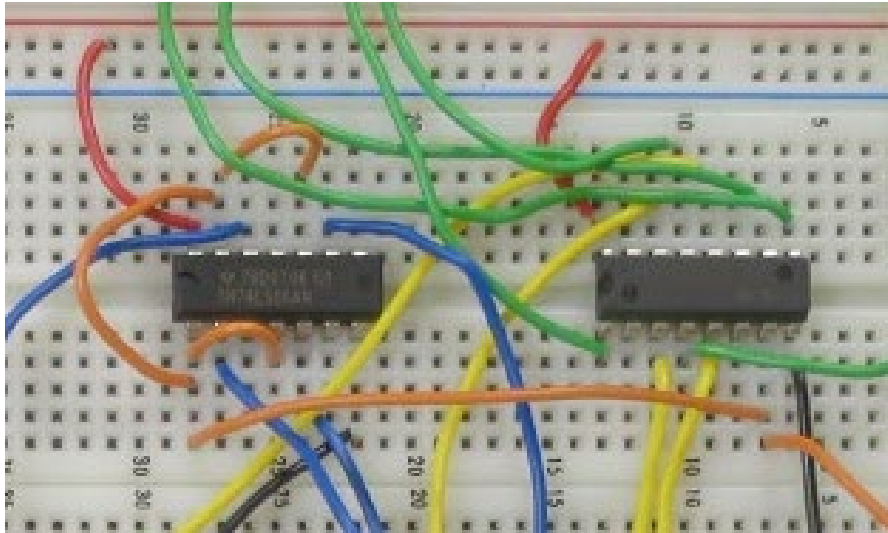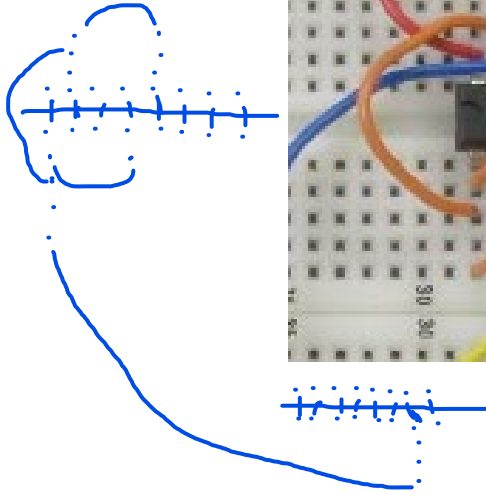9. Connect the **four remaining inputs** of the **74LS86 (quad-XOR)** to **C0 (carry input)** of the **74LS283 (4-bit adder)** (**orange wires**).



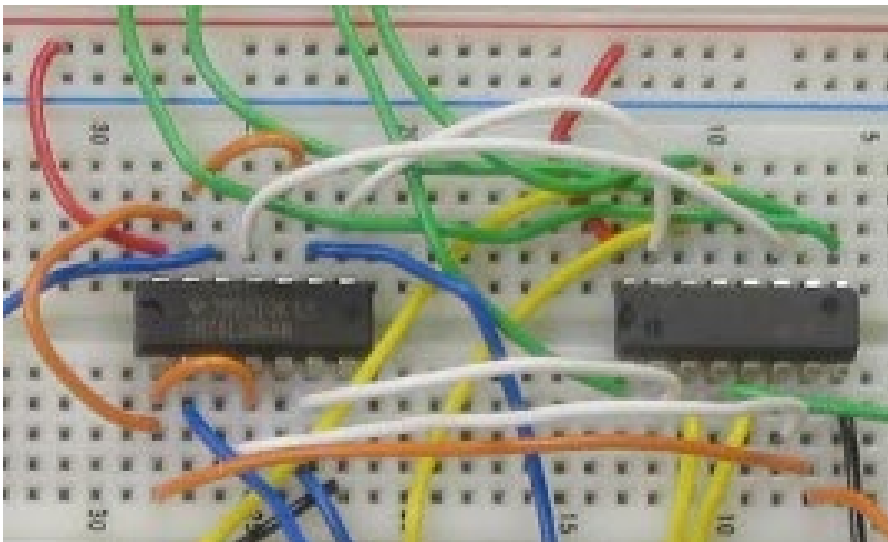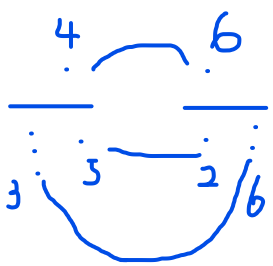10. Connect the **four outputs** of the **74LS86 (quad-XOR)** to the **B4, B3, B2 and B1 inputs** of the **74LS283 (4-bit adder)**. Make sure the order of the bits (msb to lsb) is correct (**white wires**).




DO NOT simply follow the picture above.

Make sure you have a circuit connection diagram (including pin numbers) so that you know what is connected to each pin.

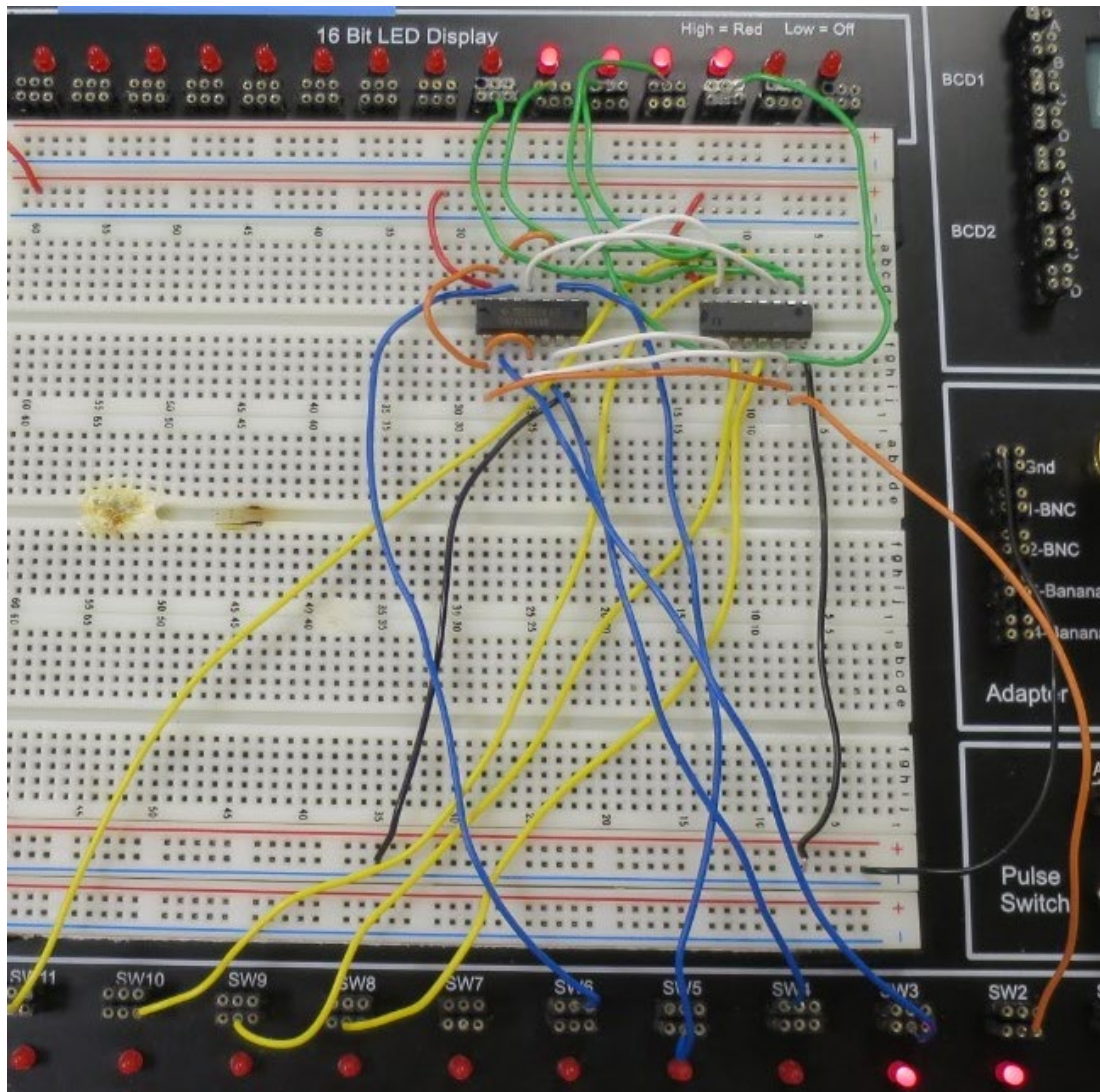11. Power up the circuit and test it out for arithmetic addition and subtraction. This figure shows the binary result of $x - y$ ($x=0000$, $y=0001$).

Outputs: C4 $\Sigma 4$ $\Sigma 3$ $\Sigma 2$ $\Sigma 1$



Inputs: x3 x2 x1 x0 y3 y2 y1 y0 Add/Sub

Example:	0 0 0 0	(0 0 0 0)	
	1 1 1 0	(Invert 0001)	} 2's complement of 0001
+	1	(Cin = 1)	
	1 1 1 1	(-1)	

End of document